

ΕΝΔΕΙΚΤΙΚΕΣ ΑΠΑΝΤΗΣΕΙΣ

Θέμα 4°

$$4.1 \quad P = U \cdot I \Rightarrow I = \frac{P}{U} \Rightarrow I = \frac{320W}{240V} \Rightarrow I = \frac{4}{3} A$$

$$4.2 \quad R_{ολ} = \frac{U}{I} \Rightarrow R_{ολ} = \frac{240V}{\frac{4}{3}A} \Rightarrow R_{ολ} = \frac{3 \cdot 240}{4} \Omega \Rightarrow R_{ολ} = 180 \Omega$$

$$R_{ολ} = R + R + R \Rightarrow R_{ολ} = 3R \Rightarrow R = \frac{R_{ολ}}{3} \Rightarrow R = \frac{180\Omega}{3} \Rightarrow R = 60 \Omega$$

$$4.3 \quad R_{ολ}' = \frac{R}{3} \Rightarrow R_{ολ}' = \frac{60\Omega}{3} \Rightarrow R_{ολ}' = 20 \Omega$$

$$4.4 \quad I' = \frac{U}{R_{ολ}'} \Rightarrow I' = \frac{240V}{20\Omega} \Rightarrow I' = 12A$$

$$4.5 \quad P' = U \cdot I' \Rightarrow P' = 240V \cdot 12A \Rightarrow P' = 2880W$$